

# PUE 3141: ADVANCED DIGITAL SYSTEMS DESIGN

## LECTURE 2

13/07/2022

BY DR. MUTUGI KIRUKI

### Topics:

- i) Combinational & Sequential Logic Designs with Verilog HDL

### References:

- i) Mano, M.M., & Ciletti, M.D. (2007) *Digital Design* (4<sup>th</sup> Edition). Pearson.

### Introduction to Verilog HDL

**Hardware Description Language (HDL):** Computer-based language that describes the hardware of digital systems in a textual form. It describes hardware structures and the behavior of logic circuits. It can be used to represent:

- Logic diagrams
- Boolean expressions
- Truth tables
- Complex abstractions of the behavior of a digital system

HDLs are used in various major steps in digital system design flow such as:

- Design entry
- Logic Synthesis
- Logic Simulation
- Timing verification & fault simulation

#### ***Design entry:***

Creates an HDL-based description of the functionality that is to be implemented in hardware. This can be in various forms such as: Boolean logic equations, truth tables, a netlist of interconnected gates, or an abstract behavioral model.

#### ***Logic simulation:***

Simulation of a circuit predicts how the hardware will behave before it is actually fabricated. This allows the detection of functional errors in a design without having to physically create and operate the circuit. Errors detected in the simulation can be corrected by modifying the appropriate HDL statements. ***Test bench*** is the stimulus (i.e., the logic values of the inputs to a circuit) that tests the functionality of the design.

#### ***Logic synthesis:***

This is the process of deriving a list of physical components and their interconnections (netlist) from the model of a digital system described in an HDL. This netlist can then be used to fabricate an IC or to lay out a PCB with the hardware counterparts of the gates in the list. Logic synthesis is similar to compiling a program in a conventional high-level language. However, instead of producing an object code, logic synthesis produces a database describing the elements and structure of a circuit. The database specifies how to fabricate a physical IC that implements in silicon the functionality described by statements made in an HDL.


### Timing verification:

Each logic gate in a circuit has a *propagation delay*, hence a signal transition at the input of a circuit cannot immediately cause a change in the logic value of the output of a circuit. Propagation delays ultimately limit the speed at which a circuit can operate. Timing verification checks each signal path to verify that it is not compromised by propagation delay.

Two standard HDLs supported by IEEE are:

- Very High Speed Integrated Circuit (VHSIC) HDL i.e., VHDL
- Verilog

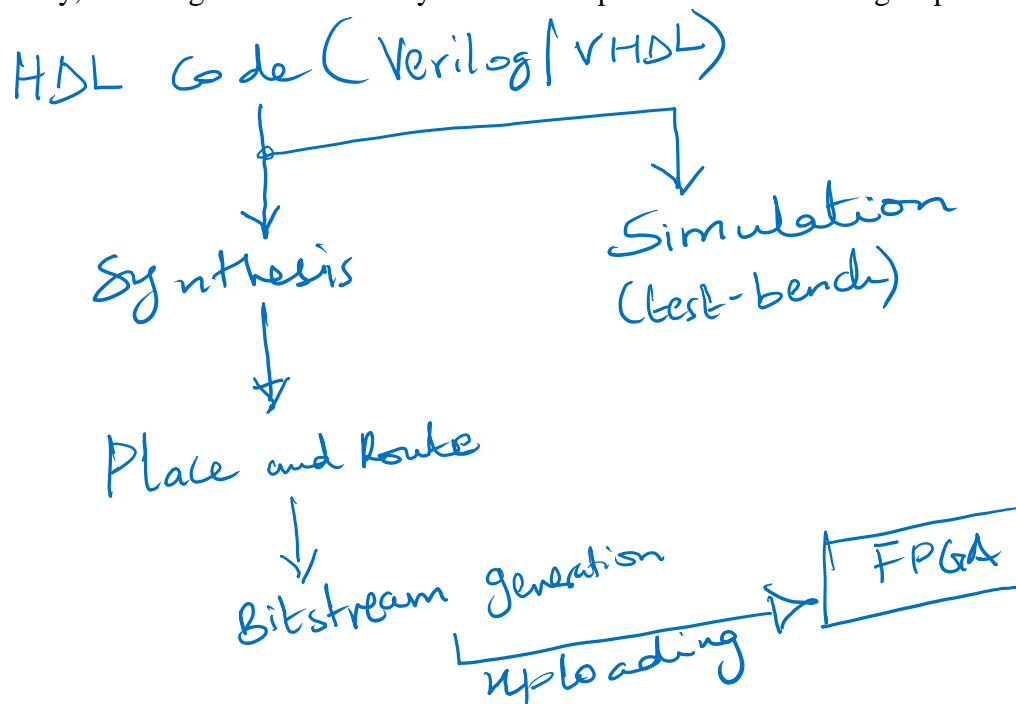Generally, the design flow in CAD systems is comprised of the following steps:



### Verilog Syntax

- Verilog is case sensitive. All Verilog keywords are lower-case
- **Number syntax:** <size>'<radix><value>;
  - Unsized numbers are stored as 32-bit e.g., 1 is stored as 32-bit
  - Radix include binary, octal, decimal, hexadecimal
  - Radix and hex digits (a,b,c,d,e,f) are case insensitive
  - When <size> is smaller than <value>, then leftmost bits of <value> are truncated

E.g.: 8'hBA, 7'b1001101, 'hFC

- **Data Types:**

Verilog has two primary data types:

- Nets: represent structural connections between components. E.g.: **wire**
- Registers: represent variables used to store data.
  - ✓ Registers store the last value assigned to them until another assignment statement changes their value. They represent data storage constructs.
  - ✓ Register Data Types:

**reg** – unsigned variable

**time** – unsigned integer (64 bits)

**integer** – signed variable (32 bits)

**real** – Double precision floating point variable

- **Verilog Operators:**

- Arithmetic Operators - Binary: +, -, \*, /, %
- Relational operators - <, >, <=, >=. The result is 0 if the relation is false and 1 if the relation is true
- Logical operators - !: logic negation, &&: logical and, ||: logical or
- Bit-wise operators - ~: negation, &: and, |: inclusive or, ^: exclusive or

- **Modules:**


A module is the fundamental descriptive unit in the Verilog language. It is declared by the keyword **module** and must always be terminated by the keyword **endmodule**.

## Combinational Logic

- Can be described by a schematic connection of gates, a set of Boolean equations, or by a truth table
 
### Example 1\_A:

- Using Icarus Verilog for HDL simulation.
- Logic described by logic diagram/schematic



A	B	C	D	E
0	0	0	1	1
0	0	1	0	0
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	1	1
1	1	1	1	0

module

inputs  $\rightarrow$  A, B, C

outputs  $\rightarrow$  D, E

wire  $\rightarrow$  w1

endmodule

## Top Module

```

module example_one (A, B, C, D, E);
//Declare inputs, outputs and internal connections
input A, B, C;
output D, E;
wire w1;

//Implementation of the circuit / schematic
and G1(w1, A, B); //Instantiate the and module
not G2(E, C);
or G3(D, w1, E);

endmodule

```

## Test Bench

```
`timescale 1ns/1ns

`include "example_one.v"

module example_one_tb;
reg A, B, C; //inputs to simulate
wire D, E;   //outputs to simulate

//Instantiate the module that we are simulating
example_one  tb_one (A, B, C, D, E); //Retain the same
order

//simulate the circuit using the initial block
initial
    begin
        $dumpfile("example_one_tb.vcd");
        $dumpvars(0,example_one_tb);
        A = 1'b0; B = 1'b0; C = 1'b0;
        #30 A = 1'b1;
        #30 A = 1'b0; B = 1'b1; C = 1'b0;
        #60 A = 1'b1; B = 1'b1; C = 1'b1;
        #30
        $display ("Simulation ended");
    end

endmodule
```

### Note:

In simulation, it's necessary to specify the propagation delay i.e. the amount of delay from the input to the output of its gates. In Verilog, the propagation delay of a gate is specified in terms of *time units* and is specified by the symbol #.

The association of a time unit with physical time is made with the '**timescale** compiler directive.


E.g. '**timescale 1ns/100ps** -> 1<sup>st</sup> value specifies the unit of measurement for time delays. The 2<sup>nd</sup> value specifies the precision for which delays are rounded off, in this case to 0.1 ns.

## Top Module with Propagation Delays

```
module example_one_prop_delay (A, B, C, D, E);  
  //Declare inputs, outputs and internal connections  
  input A, B, C;  
  output D, E;  
  wire w1;  
  
  //Implementation of the circuit / schematic  
  and # (20) G1 (w1, A, B); //Instantiate the and module  
  not # (10) G2 (E, C);  
  or # (30) G3 (D, w1, E);  
  
endmodule
```
 
### Example 1\_B:


- Logic circuit described by Boolean Equation



## Top Module

```
module example_one (A, B, C, D, E);  
  //Declare inputs, outputs and internal connections  
  input A, B, C;  
  output D, E;  
  
  //Implementation of the Boolean Equations  
  assign D = (A & B) | ~ C;  
  assign E = ~ C;  
endmodule
```

## Example 2:

 

Boolean functions

$$w_1 = ABC$$

$$w_2 = A + B + C$$

$$w_5 = AB$$

$$w_6 = AC$$

$$w_7 = BC$$

$$Y_2 = w_5 + w_6 + w_7 = AB + AC + BC$$

$$w_3 = \overline{Y_2}$$

$$w_4 = w_2 w_3 = \overline{Y_2} w_2$$

$$Y_1 = w_1 + w_4$$

	A	B	C	w <sub>1</sub>	w <sub>2</sub>	w <sub>3</sub>	w <sub>4</sub>	Y <sub>1</sub>	Y <sub>2</sub>
0	0	0	0	0	0	1	0	0	0
1	0	0	1	0	1	0	0	0	0
2	0	1	0	0	1	0	0	0	1
3	0	1	1	0	1	0	0	0	1
4	1	0	0	0	1	0	0	0	0
5	1	0	1	0	1	0	0	0	1
6	1	1	0	0	1	0	0	0	1
7	1	1	1	1	1	0	1	1	1

## Top Module

```
module example_two (A, B, C, Y1, Y2);
//Declare inputs, outputs and internal connections
input A, B, C;
output Y1, Y2;
wire w1, w2, w3, w4, w5, w6, w7;

//Implementation of the circuit / schematic
and G1(w1, A, B, C); //Instantiate the and module
or G2(w2, A, B, C);
and G3(w5, A, B);
and G4(w6, A, C);
and G5(w7, B, C);
or G6(Y2, w5, w6, w7);
not G7(w3, Y2);
and G8(w4, w2, w3);
or G9(Y1, w1, w4);

endmodule
```

## Test Bench

```
`timescale 1ns/1ns
`include "example_two.v"

module example_two_tb;
reg A, B, C; //inputs to simulate
wire Y1, Y2; //outputs to simulate

//Instantiate the module that we are simulating
example_two tb_two (A, B, C, Y1, Y2); //Retain the
same order

//simulate the circuit using the initial block
initial
begin
    $dumpfile("example_two_tb.vcd");
    $dumpvars(0,example_two_tb);
end
```



```
A = 1'b0; B = 1'b0; C = 1'b0;  
#30 B = 1'b1;  
#30 A = 1'b0; B = 1'b1; C = 1'b1;  
#30 A = 1'b1; B = 1'b1; C = 1'b0;  
#60 A = 1'b1; B = 1'b1; C = 1'b1;  
#30  
$display ("Simulation ended");  
end
```

```
endmodule
```